 


## UNIT -V


### Registers and Counters

#### A basic register


- Basic registers are easy to build. We can store multiple bits just by putting a bunch of flip-flops together!
- A 4-bit register is given below
  - This register uses D flip-flops, so it's easy to store data without worrying about flip-flop input equations
  - All the flip-flops share a common CLK and CLR signal



## Shift Registers

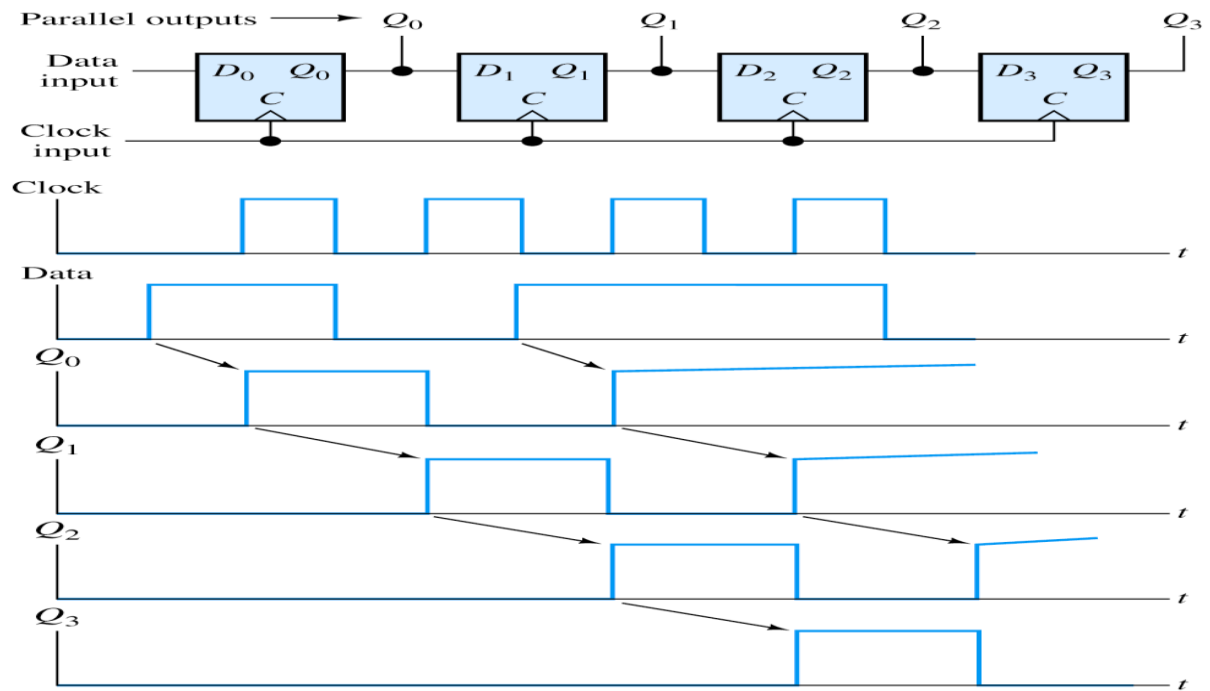


**Figure 7.48** Serial-input parallel-output shift register.

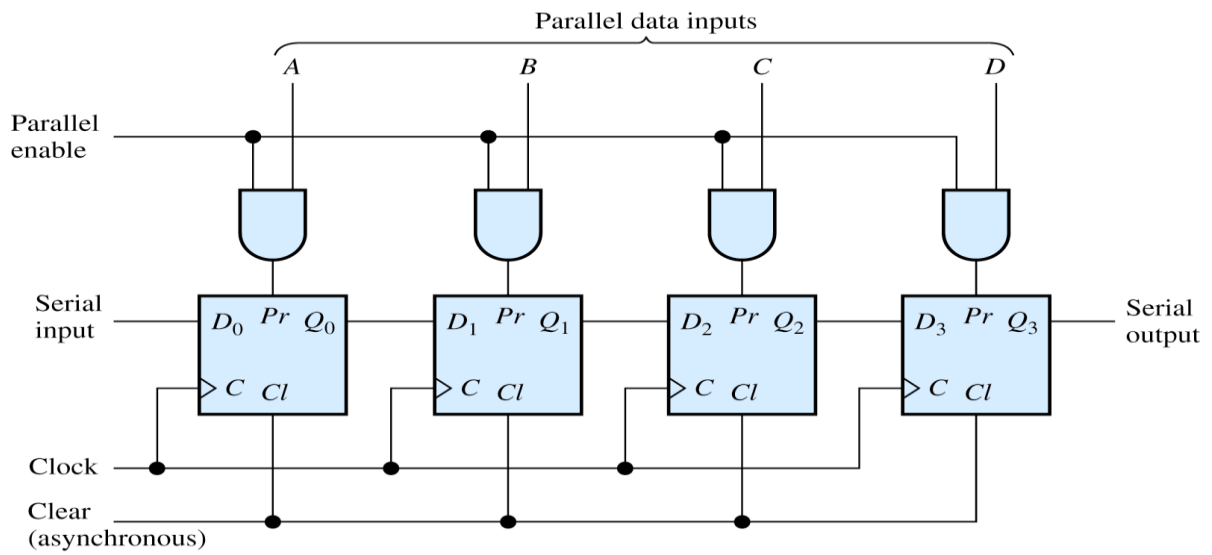

**Figure 7.49** Parallel-input serial-output shift register.

## Counters:

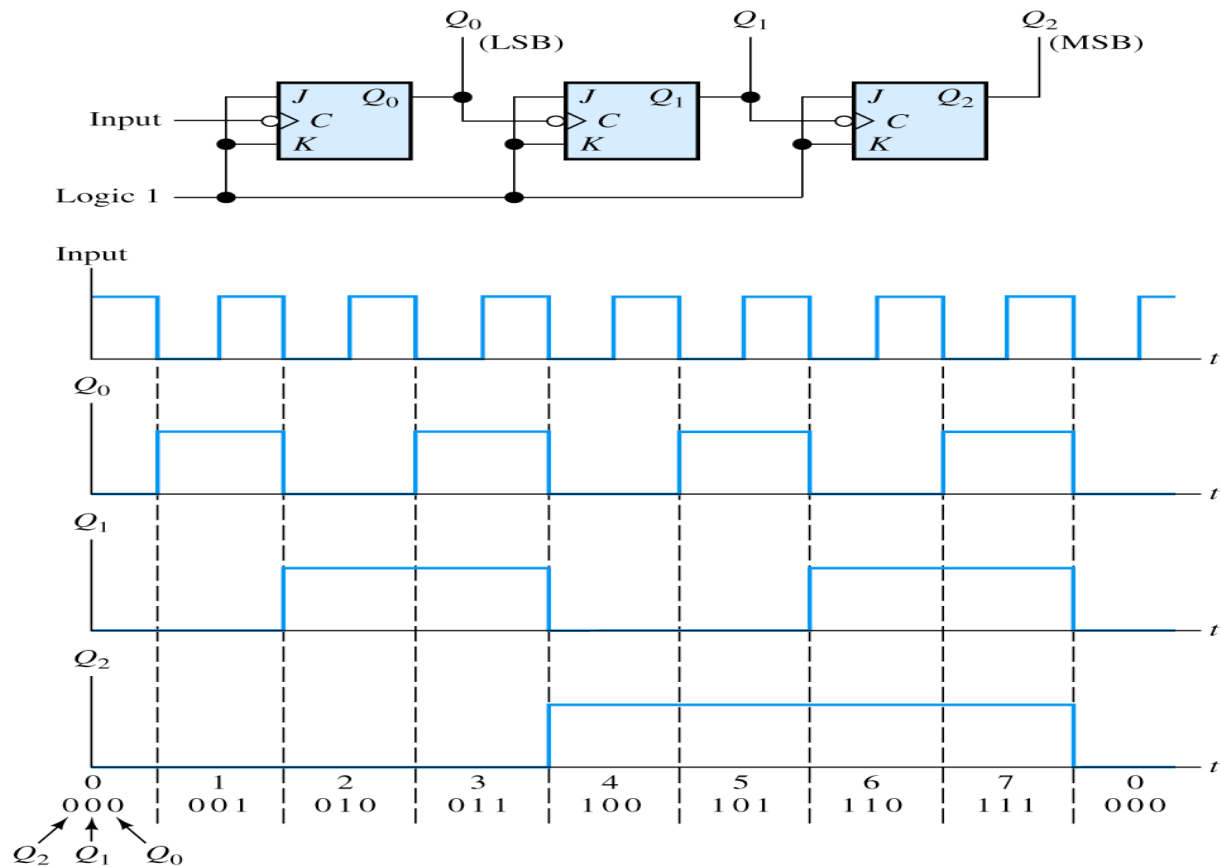

**Figure 7.50** Ripple counter.

### Introducing counters


- Counters are a specific type of sequential circuit
- The state serves as the “output” (Moore)
- A counter that follows the binary number sequence is called a binary counter
  - n-bit binary counter: n flip-flops, count in binary from 0 to  $2^n-1$
- Counters are available in two types:
  - Synchronous Counters
  - Ripple Counters
- Synchronous Counters:

A common clock signal is connected to the C input of each flip-flop
 
## Synchronous Binary Up Counter

- The output value increases by one on each clock cycle
- After the largest value, the output “wraps around” back to 0

Using two bits, we'd get something like this:




Present State		Next State	
A	B	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

### Synchronous Binary Up Counter

Present State		Next State	
A	B	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

$$D1 = A'B + AB'$$

$$DO = B'$$

 

### Synch Binary Up/Down Counter

- 2-bit Up/Down counter
  - Counter outputs will be 00, 01, 10 and 11
  - There is a single input, X.
- > X= 0, the counter counts up
- > X= 1, the counter counts down
- We'll need two flip-flops again. Here are the four possible states:

00


01

11

10
 
### The complete state diagram and table

- Here's the complete state diagram and state table for this circuit



Present State		Inputs X	Next State	
$Q_1$	$Q_0$		$Q_1$	$Q_0$
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

#### D flip-flop inputs

- If we use D flip-flops, then the D inputs will just be the same as the desired next states
- Equations for the D flip-flop inputs are shown at the right

Why does  $D_0 = Q_0'$  make sense?

Present State		Inputs	Next State	
$Q_1$	$Q_0$		$Q_1$	$Q_0$
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
$\oplus X$ 0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

			$Q_0$
	0	1	0
$Q_1$	1	0	1
		X	


$$D_1 = Q_1 \oplus Q_0$$

			$Q_0$
	1	1	0
$Q_1$	1	1	0
		X	


$$D_0 = Q_0^1$$

Synchronous Binary Up/Down Counter

## Synchronous Binary Up/Down Counter

 

## Ripple Counter

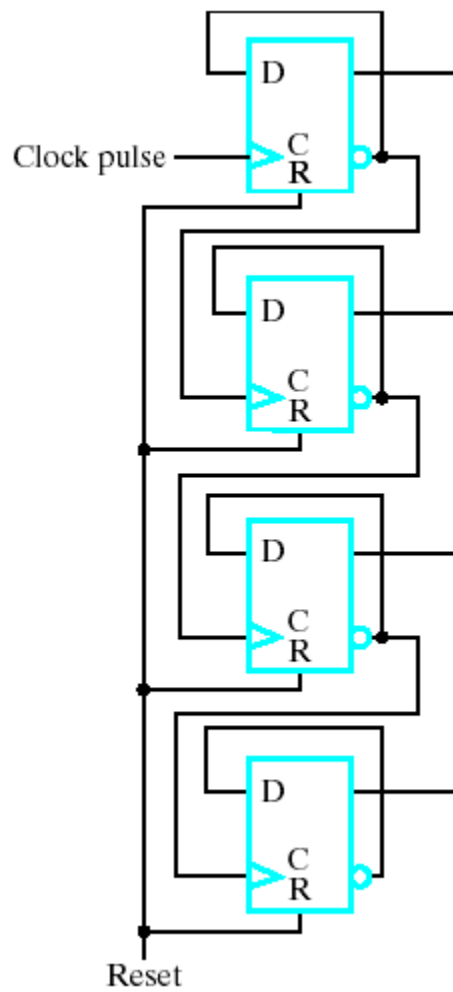

Upward Counting Sequence


$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Simple, yet asynchronous circuits ....


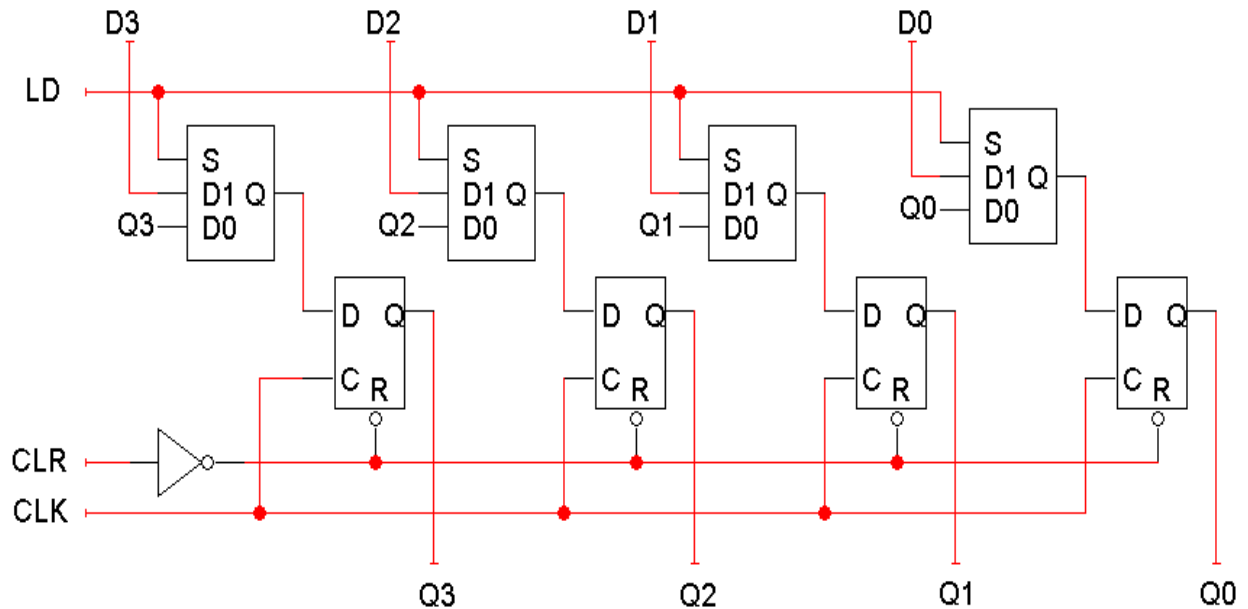
### Register with parallel load

- When  $LD = 0$ , the flip-flop inputs are  $Q_3-Q_0$ , so each flip-flop just keeps its current value
- When  $LD = 1$ , the flip-flop inputs are  $D_3-D_0$ , and this new value is “loaded” into the register.



Universal shift register:

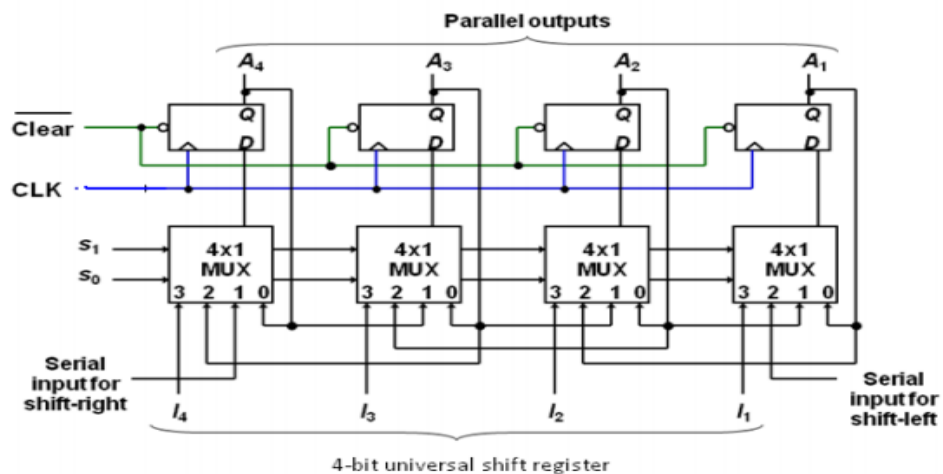


Figure: logic diagram 4-bit universal shift register

## Binary Multiplier:

+1110000

The fourth multiplier bit is a 1 write down the new multiplicand add it to the first partial product to obtain the final product.

1111110

This multiplication process can be performed by the serial multiplier circuit, which multiplies two 4-bit numbers to produce an 8-bit product. The circuit consists of following elements

**X register:** A 4-bit shift register that stores the multiplier --- it will shift right on the falling edge of the clock. Note that 0s are shifted in from the left.

**B register:** An 8-bit register that stores the multiplicand; it will shift left on the falling edge of the clock. Note that 0s are shifted in from the right.

**A register:** An 8-bit register, i.e., the accumulator that accumulates the partial products.

**Adder:** An 8-bit parallel adder that produces the sum of A and B registers. The adder outputs  $S_7$  through  $S_0$  are connected to the D inputs of the accumulator so that the sum can be transferred to the accumulator only when a clock pulse gets through the AND gate.

The circuit operation can be described by going through each step in the multiplication of 1110 by 1001. The complete process requires 4 clock cycles.

**1. Before the first clock pulse:** Prior to the occurrence of the first clock pulse, the register A is loaded with 00000000, the register B with the multiplicand 00001110, and the register X with the multiplier 1001. Assume that each of these registers is loaded using its asynchronous inputs (i.e., PRESET and CLEAR). The output of the adder will be the sum of A and B, i.e., 00001110.

**2. First Clock pulse:** Since the LSB of the multiplier ( $X_0$ ) is a 1, the first clock pulse gets through the AND gate and its positive going transition transfers the sum outputs into the accumulator. The subsequent negative going transition causes the X and B registers to shift right and left, respectively. This produces a new sum of A and B.

**3. Second Clock Pulse:** The second bit of the original multiplier is now in  $X_0$ . Since this bit is a 0, the second clock pulse is inhibited from reaching the accumulator. Thus, the sum outputs are not transferred into the accumulator and the number in the accumulator does not change. The negative going transition of the clock pulse will again shift the X and B registers. Again a new sum is produced.

**4. Third Clock Pulse:** The third bit of the original multiplier is now in  $X_0$ ; since this bit is a 0, the third clock pulse is inhibited from reaching the accumulator. Thus, the sum outputs are not transferred into the accumulator and the number in the accumulator does not change. The negative going transition of the clock pulse will again shift the X and B registers. Again a new sum is produced.

**5. Fourth Clock Pulse:** The last bit of the original multiplier is now in  $X_0$ , and since it is a 1, the positive going transition of the fourth pulse transfers the sum into the accumulator. The accumulator now holds the final product. The negative going transition of the clock pulse shifts X and B again. Note that, X is now 0000, since all the multiplier bits have been shifted out.

## Binary Multipliers:

In binary multiplication by the paper and pencil method, is modified somewhat in digital machines because a binary adder can add only two binary numbers at a time.

In a binary multiplier, instead of adding all the partial products at the end, they are added two at a time and their sum accumulated in a register (the accumulator register). In addition, when the multiplier bit is a 0, 0s are not written down and added because it does not affect the final result. Instead, the multiplicand is shifted left by one bit.

The multiplication of 1110 by 1001 using this process is

Multiplicand 1110


Multiplier 1001

1110

The LSB of the multiplier is a 1; write down the multiplicand; shift the multiplicand one position to the left (1 1 1 0 0)

1110

The second multiplier bit is a 0; write down the previous result 1110; shift the multiplicand to the left again (1 1 1 0 0 0)

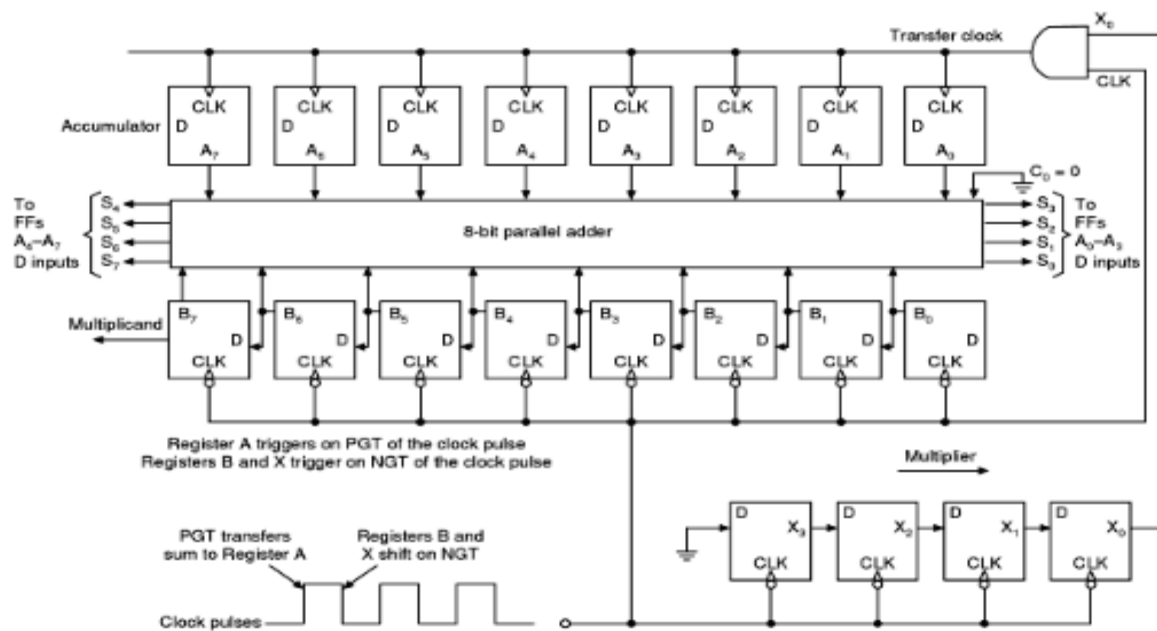

**Figure 4.31** Logic diagram of a binary multiplier.

THE END

(.....The end of education is character.....)